

**N.G.M.COLLEGE (AUTONOMOUS) : POLLACHI****END-OF-SEMESTER EXAMINATIONS : NOVEMBER – 2023****B.Sc. – PHYSICS****MAXIMUM MARKS: 70****SEMESTER: V****TIME : 3 HOURS****PART – III****BASIC ELECTRONICS AND CIRCUIT SYSTEMS****SECTION – A****(10 X 1 = 10 MARKS)****ANSWER THE FOLLOWING QUESTIONS.****MULTIPLE CHOICE QUESTIONS.****(K1)**

1. Kirchoff's voltage law is connected with
 

a. IR drops	b. battery EMFs
c. junction voltage	d. both a and b
2. When used in a circuit, the zener diode is always
 

a. forward biased	b. connected in series
c. troubled by over heating	d. reverse - biased
3. Negative feed back also referred as
 

a. Oscillator	b. regenerative feedback
c. degenerative feedback	d. clippers
4. An ideal OP-Amp has
 

a. infinite Av	b. zero Av	c. infinite Ro	d. zero Ri
----------------	------------	----------------	------------
5. The colour of light emitted by a LED depends on
 

a. its forward bias	b. the type of semiconductor material used
c. its reverse bias	d. forward current

**ANSWER THE FOLLOWING IN ONE (OR) TWO SENTENCES.****(K2)**

6. State maximum power transfer theorem.
7. What are the components used in clipping circuit?
8. Name any one of the multistage amplifier.
9. Mention any two applications of an OP-Amp
10. What is lumen?

**(CONTD .... 2)**

**SECTION – B (5 X 4 = 20 MARKS)****ANSWER EITHER (a) OR (b) IN EACH OF THE FOLLOWING QUESTIONS. (K3)**

11. a) State and explain kirchhoffs current and voltage laws. **(OR)**  
 b) Describe the RMS value of Power . Write the expression for “form factor” and “crest or peak factor”

12. a) Draw the circuit diagram for full wave rectifier and explain its working with output response curve. **(OR)**  
 b) What is Zener diode? Explain the forward and reverse bias characteristics of a Zener diode with graph.

13. a) Draw the circuit diagram for common emitter single stage amplifier and explain its operation. **(OR)**  
 b) Discuss the essentials of feedback LC oscillator and deduce the Barkhausan criterion for steady level of oscillation.

14. a) List any four characteristics of an ideal Op-Amp with definition. **(OR)**  
 b) Give the subtractor diagram using Op-amp and deduce its output expression.

15. a) Explain the principle of the light beam detector. **(OR)**  
 b) Write short note on speed response of a photo detector.

**SECTION - C****(4 X 10 = 40 MARKS)****ANSWER ANY FOUR OUT OF SIX QUESTIONS****(16<sup>th</sup> QUESTION IS COMPULSORY AND ANSWER ANY THREE QUESTIONS (FROM Qn. No : 17 to 21) (K4 (Or) K5)**

16. What is JFET? Describe its construction details and working with input and output characteristics curve.

17. Write Thevenin’s theorm . Give the steps involved in Thevenizing a circuit.

18. Draw the circuit diagram for common emitter configuration of a transistor and explain its working with input and out put characteristic curves. .

19. With circuit diagram explain the working of colpitt’s oscillator give some of its applications.

20. Explain the functions of the inverting and non inverting configurations of an Op-amp with circuits and gain expressions.

21. Give the theory of Light Emitting diode. Explain the construction and functions of LED with its features. Mention any five applications of LED.