

(FOR THE CANDIDATES ADMITTED SUBJECT CODE **23 UMS 4A4 / 23UCY4A5**
 DURING THE ACADEMIC YEAR 2023-24 ONLY) REG.NO. _____

N.G.M.COLLEGE (AUTONOMOUS) : POLLACHI

END-OF-SEMESTER EXAMINATIONS : MAY- 2025

B.Sc. – MATHEMATICS / CHEMISTRY

MAXIMUM MARKS: 75

IV SEMESTER

TIME : 3 HOURS

PART – III

ANCILLARY PHYSICS FOR MATHEMATICS AND CHEMISTRY-II
SECTION – A (10 X 1 = 10 MARKS)

ANSWER THE FOLLOWING QUESTIONS.

(K1)

1. The device utilized to measure potential difference is
 a) magnetometer b) zener diode c) ammeter d) voltmeter
2. The phenomenon observed in Young's double slit experiment is
 a) polarization b) diffraction c) interference d) rectilinear propagation
3. Which one of the following is unidirectional device ?
 a) transistor b) Zener diode c) junction diode d) capacitor
4. Sum of opaque and transparent region in a grating is called as
 a) grating element b) corresponding region c) bandwidth d) grating wavelength
5. The NOR gate is ON only when all its inputs are
 a) ON b) positive c) high d) OFF

ANSWER THE FOLLOWING IN ONE (OR) TWO SENTENCES.

(K2)

6. State "Kirchoff's second law".
7. What is circular polarization?
8. What is the application of a rectifier?
9. What are known as excess 3 code?
10. Give the truth table of XOR gate.

SECTION – B (5 X 5 = 25 MARKS)

ANSWER EITHER (a) OR (b) IN EACH OF THE FOLLOWING QUESTIONS.
(K3)

11. a) Obtain an expression for Energy Stored in a charged capacitor.
 (OR)
 b) Draw the diagram of potentiometer and describe its construction and uses.
12. a) How do interference fringes are formed? Explain it theory.
 (OR)
 b) Define the term dispersive power of the prism. Deduce an expression for it.

(CONTD 2)

13. a) Draw the circuit diagram for full wave rectifier and describe its working.
(OR)
b) Describe the action of the transistor with its construction details.

14. a) Convert the following binary operations
i) 1100×101 (2marks) ii) $101011 - 10010$ (2marks) iii) $1011 + 1001$ (1 mark)
(OR)

b) Write a note on ASCII codes

15. a) State and prove Demorgan's theorem.
(OR)
b) Construct OR and AND gates using discrete components and describe its working with truth tables.

SECTION – C (5 X 8 = 40 MARKS)

ANSWER EITHER (a) OR (b) IN EACH OF THE FOLLOWING QUESTIONS.
(K4 (Or) K5)